

Міністерство освіти і науки України  
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 3

з дисципліни «Моделювання комп'ютерних систем»  
на тему:

«Поведінковий опис цифрового автомата Перевірка роботи автомата за  
допомогою стенда Elbert V2 – Spartan 3A FPGA»


Варіант №17

Виконав:  
ст. гр. КІ-201  
Курило А.О.  
Прийняв:  
ст. викладач  
каф. ЕОМ  
Козак Н. Б.

Львів 2024

**Мета роботи:** На базі стенда реалізувати цифровий автомат для обчислення значення виразів.

### Виконання роботи:

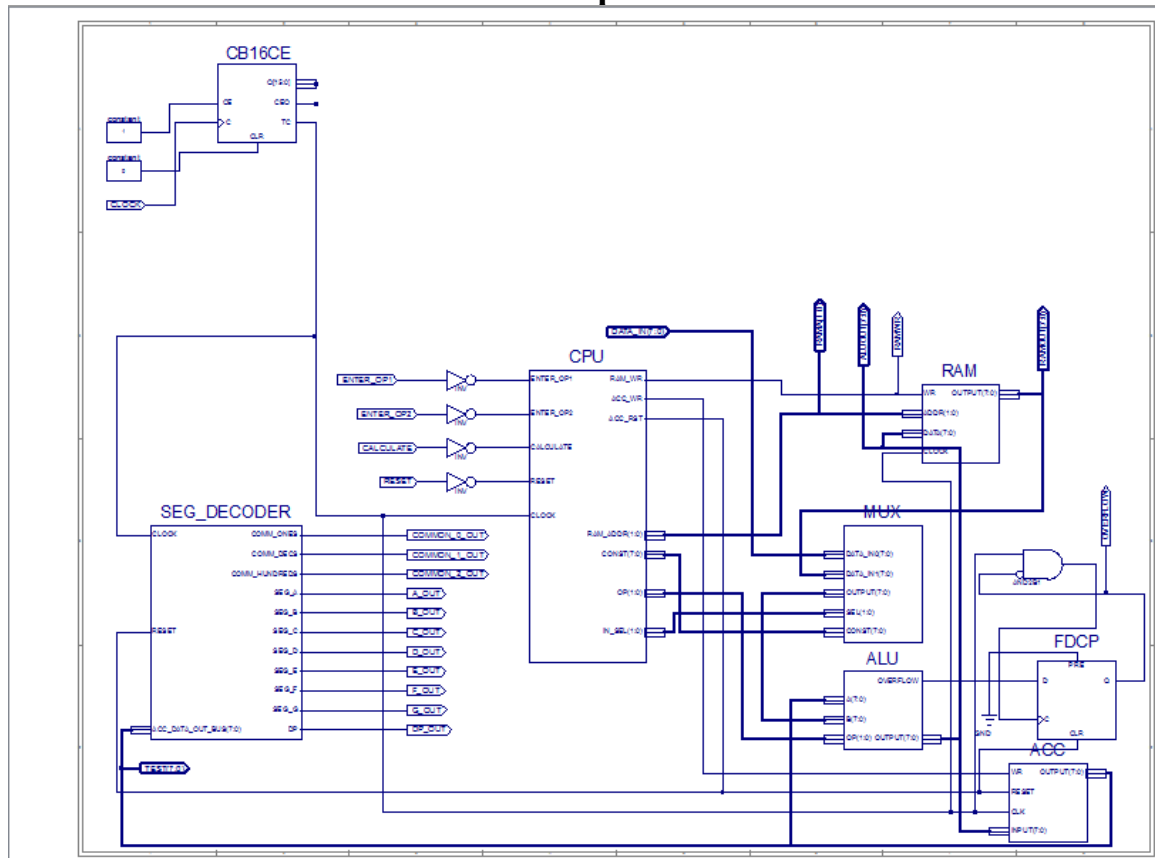

*Рис. 1 – Top Level*

Файл ACC.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

entity ACC is

```
    Port ( WR : in STD_LOGIC;
          RESET : in STD_LOGIC;
          CLK : in STD_LOGIC;
          INPUT : in STD_LOGIC_VECTOR (7 downto 0);
          OUTPUT : out STD_LOGIC_VECTOR (7 downto 0));
```

end ACC;

architecture ACC\_arch of ACC is

```
    signal DATA : STD_LOGIC_VECTOR (7 downto 0);
begin
```

```

process (CLK)
begin
    if rising_edge(CLK) then
        if RESET = '1' then
            DATA <= (others => '0');
        elsif WR = '1' then
            DATA <= INPUT;
        end if;
    end if;
end process;

OUTPUT <= DATA;

end ACC_arch;

```

```

Файл ALU.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ALU is
    Port ( A : in  STD_LOGIC_VECTOR(7 downto 0);
          B : in  STD_LOGIC_VECTOR(7 downto 0);
          OP : in  STD_LOGIC_VECTOR(1 downto 0);
          OUTPUT : out STD_LOGIC_VECTOR(7 downto 0);
          OVERFLOW: out STD_LOGIC);
end ALU;

architecture ALU_Behavioral of ALU is
    signal ALUR: STD_LOGIC_VECTOR(15 downto 0) := (others => '0');
    signal Carry: STD_LOGIC := '0';
begin
    process(A, B, OP)
    begin
        case (OP) is
            when "01" => ALUR <= ("00000000" & A) +
("00000000" & B);
            when "10" => ALUR <= ("00000000" & A) and
("00000000" & B);

```

```

        when "11" => case(B) is
            when x"00"      => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) sll 0);
            when x"01"      => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) sll 1);
            when x"02"      => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) sll 2);
            when x"03"      => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) sll 3);
            when x"04"      => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) sll 4);
            when x"05"      => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) sll 5);
            when x"06"      => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) sll 6);
            when x"07"      => ALUR <=
std_logic_vector(unsigned(("00000000" & A)) sll 7);
            when others => ALUR <= (others => '0');
        end case;
        ALUR(15 downto 8) <= "00000000";
        when others => ALUR <= ("00000000" & B);
    end case;
end process;
OUTPUT <= ALUR(7 downto 0);
OVERFLOW <= ALUR(8) OR ALUR(9) OR ALUR(10) OR
ALUR(11) OR ALUR(12) OR ALUR(13) OR ALUR(14) OR ALUR(15);
end ALU_Behavioral;

```

Файл CPU.vhd

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity CPU is

port( ENTER\_OP1 : IN STD\_LOGIC;

ENTER\_OP2 : IN STD\_LOGIC;

CALCULATE : IN STD\_LOGIC;

RESET : IN STD\_LOGIC;

CLOCK : IN STD\_LOGIC;

RAM\_WR : OUT STD\_LOGIC;

RAM\_ADDR : OUT STD\_LOGIC\_VECTOR(1

DOWNT0 0);

CONST : OUT STD\_LOGIC\_VECTOR(7 DOWNT0 0);

```

        ACC_WR : OUT STD_LOGIC;
        ACC_RST : OUT STD_LOGIC;
        IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);
        OP : OUT STD_LOGIC_VECTOR(1 DOWNT0 0));
end CPU;

architecture CPU_arch of CPU is

type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2,
RUN_CALC0, RUN_CALC1, RUN_CALC2, RUN_CALC3, RUN_CALC4,
FINISH);
signal CUR_STATE : STATE_TYPE;
signal NEXT_STATE : STATE_TYPE;

begin
    SYNC_PROC: process (CLOCK)
    begin
        if (rising_edge(CLOCK)) then
            if (RESET = '1') then
                CUR_STATE <= RST;
            else
                CUR_STATE <= NEXT_STATE;
            end if;
        end if;
    end process;

    NEXT_STATE_DECODE: process (CLOCK, ENTER_OP1,
ENTER_OP2, CALCULATE)
    begin
        NEXT_STATE <= CUR_STATE;

        case(CUR_STATE) is
            when RST =>
                NEXT_STATE <= IDLE;
            when IDLE =>
                if (ENTER_OP1 = '1') then
                    NEXT_STATE <= LOAD_OP1;
                elsif (ENTER_OP2 = '1') then
                    NEXT_STATE <= LOAD_OP2;
                elsif (CALCULATE = '1') then
                    NEXT_STATE <= RUN_CALC0;
                else

```

```

        NEXT_STATE <= IDLE;
    end if;
    when LOAD_OP1 =>
        NEXT_STATE <= IDLE;
    when LOAD_OP2 =>
        NEXT_STATE <= IDLE;
    when RUN_CALC0 =>
        NEXT_STATE <= RUN_CALC1;
    when RUN_CALC1 =>
        NEXT_STATE <= RUN_CALC2;
    when RUN_CALC2 =>
        NEXT_STATE <= RUN_CALC3;
    when RUN_CALC3 =>
        NEXT_STATE <= RUN_CALC4;
    when RUN_CALC4 =>
        NEXT_STATE <= FINISH;
    when FINISH =>
        NEXT_STATE <= FINISH;
    when others =>
        NEXT_STATE <= IDLE;
    end case;
end process;

```

OUTPUT\_DECODE: process (CUR\_STATE)

begin

case (CUR\_STATE) is

when RST =>

RAM\_WR <= '0';

RAM\_ADDR <= "00";

CONST <= "00000000";

ACC\_WR <= '0';

ACC\_RST <= '1';

IN\_SEL <= "00";

OP <= "00";

when LOAD\_OP1 =>

RAM\_WR <= '1';

RAM\_ADDR <= "00";

CONST <= "00000000";

ACC\_WR <= '0';

ACC\_RST <= '1';

IN\_SEL <= "00";

OP <= "00";

when LOAD\_OP2 =>

```

        RAM_WR <= '1';
        RAM_ADDR <= "01";
        CONST <= "00000000";
        ACC_WR <= '0';
        ACC_RST <= '1';
        IN_SEL <= "00";
        OP <= "00";
when RUN_CALC0 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000001";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "00";
when RUN_CALC1 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "11";
when RUN_CALC2 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "01";
when RUN_CALC3 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00001010";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "01";
when RUN_CALC4 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000000";

```

```

        ACC_WR <= '1';
        ACC_RST <= '0';
        IN_SEL <= "01";
        OP <= "10";
    when IDLE =>
        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "00000000";
        ACC_WR <= '0';
        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "00";
    when others =>
        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "00000000";
        ACC_WR <= '0';
        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "00";
    end case;
end process;
end CPU_arch;

```

Файл FullAdder.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity FullAdder is
    Port (A: in STD_LOGIC;
          B: in STD_LOGIC;
          Ci: in STD_LOGIC;
          S: out STD_LOGIC;
          Co: out STD_LOGIC);
end FullAdder;

architecture Behavioral of FullAdder is
begin
    S <= (A xor B) xor Ci;
    Co <= (A and B) or ((A xor B) and Ci);
end Behavioral;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```



```

entity FullAdder8 is
  Port ( A: in STD_LOGIC_VECTOR (7 downto 0);
        B: in STD_LOGIC_VECTOR (7 downto 0);
        Ci: in STD_LOGIC;
        S: out STD_LOGIC_VECTOR (7 downto 0);
        Co: out STD_LOGIC);
end FullAdder8;

architecture Behavioral of FullAdder8 is
  component FullAdder is
    Port (A: in STD_LOGIC;
          B: in STD_LOGIC;
          Ci: in STD_LOGIC;
          S: out STD_LOGIC;
          Co: out STD_LOGIC);
  end component;
  signal carry: STD_LOGIC_VECTOR(8 downto 0) := (others =>
'0');
begin
  carry(0) <= Ci;
  FullAdderGenerate: for i in 0 to 7 generate
    adder: FullAdder port map(
      A => A(i),
      B => B(i),
      Ci => carry(i),
      S => S(i),
      Co => carry(i + 1)
    );
  end generate FullAdderGenerate;
  Co <= carry(8);
end Behavioral;

```

Файл MUX.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX is
  PORT(
    SEL: in STD_LOGIC_VECTOR(1 downto 0);
    CONST: in STD_LOGIC_VECTOR(7 downto 0);
    --CONST1: in STD_LOGIC_VECTOR()
    DATA_IN0: in STD_LOGIC_VECTOR(7 downto 0);
    DATA_IN1: in STD_LOGIC_VECTOR(7 downto 0);

```

```

        OUTPUT: out STD_LOGIC_VECTOR(7 downto 0)
    );
end MUX;

architecture Behavioral of MUX is
begin
    process (SEL, DATA_IN0, DATA_IN1, CONST)
    begin
        if (SEL = "00") then
            OUTPUT <= DATA_IN0;
        elsif (SEL = "01") then
            OUTPUT <= DATA_IN1;
        else
            OUTPUT <= CONST;
        end if;
    end process;
end Behavioral;

```

```

Файл RAM.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity RAM is
    port(
        WR : IN STD_LOGIC;
        ADDR : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        DATA : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        CLOCK: IN STD_LOGIC;
        OUTPUT : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
end RAM;

architecture RAM_arch of RAM is
    type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7
downto 0);
    signal UNIT : ram_type;

begin
    process(ADDR, CLOCK, UNIT)

```

```

begin
    if(rising_edge(CLOCK)) then
        if (WR = '1') then
            UNIT(conv_integer(ADDR)) <= DATA;
        end if;
    end if;
    OUTPUT <= UNIT(conv_integer(ADDR));
end process;
end RAM_arch;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity SEG_DECODER is
    port( CLOCK : IN STD_LOGIC;
          RESET : IN STD_LOGIC;
          ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7
DOWNTO 0);
          COMM_ONES          : OUT STD_LOGIC;
          COMM_DECS          : OUT STD_LOGIC;
          COMM_HUNDREDS     : OUT STD_LOGIC;
          SEG_A      : OUT STD_LOGIC;
          SEG_B      : OUT STD_LOGIC;
          SEG_C      : OUT STD_LOGIC;
          SEG_D      : OUT STD_LOGIC;
          SEG_E      : OUT STD_LOGIC;
          SEG_F      : OUT STD_LOGIC;
          SEG_G      : OUT STD_LOGIC;
          DP          : OUT STD_LOGIC);
end SEG_DECODER;

architecture Behavioral of SEG_DECODER is

    signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
    signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
    signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) :=
"0000";

begin

```

```

    BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
    variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
    variable bcd     : STD_LOGIC_VECTOR(11 downto 0) ;
begin
    bcd      := (others => '0') ;
    hex_src  := ACC_DATA_OUT_BUS;

    for i in hex_src'range loop
        if bcd(3 downto 0) > "0100" then
            bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
        end if ;
        if bcd(7 downto 4) > "0100" then
            bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
        end if ;
        if bcd(11 downto 8) > "0100" then
            bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
        end if ;

        bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new
entry
        hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; --
shift src + pad with 0
    end loop ;

    HONDREDS_BUS  <= bcd (11 downto 8);
    DECS_BUS      <= bcd (7 downto 4);
    ONES_BUS      <= bcd (3 downto 0);

end process BIN_TO_BCD;

INDICATE : process(CLOCK)
    type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

    variable CUR_DIGIT    : DIGIT_TYPE := ONES;
    variable DIGIT_VAL    : STD_LOGIC_VECTOR(3 downto 0)
:= "0000";
    variable DIGIT_CTRL   : STD_LOGIC_VECTOR(6 downto 0)
:= "00000000";
    variable COMMONS_CTRL : STD_LOGIC_VECTOR(2
downto 0) := "000";

    begin
        if (rising_edge(CLOCK)) then

```

```

if(RESET = '0') then
  case CUR_DIGIT is
    when ONES =>
      DIGIT_VAL := ONES_BUS;
      CUR_DIGIT := DECS;
      COMMONS_CTRL := "001";
    when DECS =>
      DIGIT_VAL := DECS_BUS;
      CUR_DIGIT := HUNDREDS;
      COMMONS_CTRL := "010";
    when HUNDREDS =>
      DIGIT_VAL :=
HONDREDS_BUS;

      CUR_DIGIT := ONES;
      COMMONS_CTRL := "100";
    when others =>
      DIGIT_VAL := ONES_BUS;
      CUR_DIGIT := ONES;
      COMMONS_CTRL := "000";
  end case;

  case DIGIT_VAL is      --abcdefg
    when "0000" => DIGIT_CTRL :=
"1111110";
    when "0001" => DIGIT_CTRL :=
"0110000";
    when "0010" => DIGIT_CTRL :=
"1101101";
    when "0011" => DIGIT_CTRL :=
"1111001";
    when "0100" => DIGIT_CTRL :=
"0110011";
    when "0101" => DIGIT_CTRL :=
"1011011";
    when "0110" => DIGIT_CTRL :=
"1011111";
    when "0111" => DIGIT_CTRL :=
"1110000";
    when "1000" => DIGIT_CTRL :=
"1111111";
    when "1001" => DIGIT_CTRL :=
"1111011";

```

```

when others => DIGIT_CTRL :=
"0000000";

        end case;
    else
        DIGIT_VAL := ONES_BUS;
        CUR_DIGIT := ONES;
        COMMONS_CTRL := "000";
    end if;

    COMM_ONES    <= not COMMONS_CTRL(0);
    COMM_DECS    <= not COMMONS_CTRL(1);
    COMM_HUNDREDS <= not
COMMONS_CTRL(2);

    SEG_A <= not DIGIT_CTRL(6);
    SEG_B <= not DIGIT_CTRL(5);
    SEG_C <= not DIGIT_CTRL(4);
    SEG_D <= not DIGIT_CTRL(3);
    SEG_E <= not DIGIT_CTRL(2);
    SEG_F <= not DIGIT_CTRL(1);
    SEG_G <= not DIGIT_CTRL(0);
    DP    <= '1';

    end if;
end process INDICATE;

end Behavioral;

```

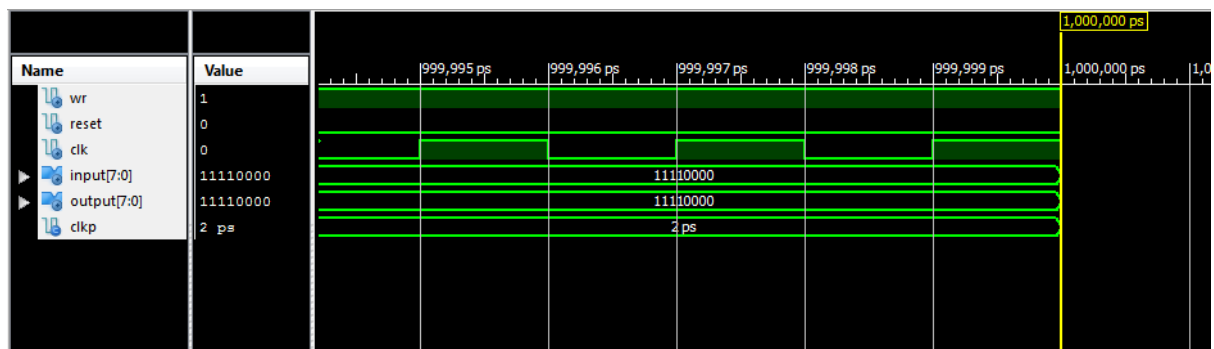


Рис. 2 – Часова діаграма АСС

 


Рис. 3 – Часова діаграма ALU

 


Рис. 4 – Часова діаграма MUX

 


Рис. 5 – Часова діаграма RAM

 


Рис 6. – Часова діаграма SEG\_DECODER



Рис 7. – Часова діаграма TopLevel

*Файл TopLevelTest.vhd*

*LIBRARY ieee;*

*USE ieee.std\_logic\_1164.ALL;*

*USE ieee.numeric\_std.ALL;*

*LIBRARY UNISIM;*

*USE UNISIM.Vcomponents.ALL;*

*ENTITY TopLevel\_TopLevel\_sch\_tb IS*

*END TopLevel\_TopLevel\_sch\_tb;*

*ARCHITECTURE behavioral OF TopLevel\_TopLevel\_sch\_tb IS*

*COMPONENT TopLevel*

*PORT( CLOCK : IN STD\_LOGIC;*

*RESET : IN STD\_LOGIC;*

*ENTER\_OP1 : IN STD\_LOGIC;*

*ENTER\_OP2 : IN STD\_LOGIC;*

*CALCULATE : IN STD\_LOGIC;*

*DATA\_IN : IN STD\_LOGIC\_VECTOR (7 DOWNT0 0);*

*COMMON\_0\_OUT : OUT STD\_LOGIC;*

*COMMON\_1\_OUT : OUT STD\_LOGIC;*

*COMMON\_2\_OUT : OUT STD\_LOGIC;*

*TEST: OUT STD\_LOGIC\_VECTOR(7 downto 0);*

*A\_OUT : OUT STD\_LOGIC;*

*B\_OUT : OUT STD\_LOGIC;*

*C\_OUT : OUT STD\_LOGIC;*

*D\_OUT : OUT STD\_LOGIC;*

*E\_OUT : OUT STD\_LOGIC;*

*F\_OUT : OUT STD\_LOGIC;*

*G\_OUT : OUT STD\_LOGIC;*

*DP\_OUT : OUT STD\_LOGIC;*

*RAMOUT: OUT STD\_LOGIC\_VECTOR(7 downto 0);*

*ALUOUT: OUT STD\_LOGIC\_VECTOR(7 downto 0);*

*RAMA: OUT STD\_LOGIC\_VECTOR(1 downto 0);*

*RAMWR: OUT STD\_LOGIC;*

*OVERFLOW : OUT STD\_LOGIC);*

*END COMPONENT;*

*SIGNAL CLOCK : STD\_LOGIC := '0';*

*SIGNAL RESET : STD\_LOGIC;*

*SIGNAL ENTER\_OP1 : STD\_LOGIC;*

*SIGNAL ENTER\_OP2 : STD\_LOGIC;*

*SIGNAL CALCULATE : STD\_LOGIC;*

*SIGNAL DATA\_IN : STD\_LOGIC\_VECTOR (7 DOWNT0 0);*



```

SIGNAL COMMON_0_OUT :    STD_LOGIC;
SIGNAL COMMON_1_OUT :    STD_LOGIC;
SIGNAL COMMON_2_OUT :    STD_LOGIC;
SIGNAL A_OUT:          STD_LOGIC;
SIGNAL B_OUT:          STD_LOGIC;
SIGNAL C_OUT:          STD_LOGIC;
SIGNAL D_OUT          :    STD_LOGIC;
SIGNAL E_OUT:          STD_LOGIC;
SIGNAL F_OUT:          STD_LOGIC;
SIGNAL G_OUT          :    STD_LOGIC;
SIGNAL DP_OUT          :    STD_LOGIC;
SIGNAL OVERFLOW :      STD_LOGIC;
    SIGNAL TEST: STD_LOGIC_VECTOR(7 downto 0);
    SIGNAL TEST2: STD_LOGIC_VECTOR(7 downto 0);
    signal RAMOUT: STD_LOGIC_VECTOR(7 downto 0);
    signal ALUOUT: STD_LOGIC_VECTOR(7 downto 0);
    signal RAMA: STD_LOGIC_VECTOR(1 downto 0);
    signal RAMWR: STD_LOGIC;

--    constant CLOCK_period : time := 166ns;
    constant CLKP: time := 12ms;--24ms;

```

**BEGIN**

```

    UUT: TopLevel PORT MAP(
        CLOCK => CLOCK,
        RESET => RESET,
        ENTER_OP1 => ENTER_OP1,
        ENTER_OP2 => ENTER_OP2,
        CALCULATE => CALCULATE,
        DATA_IN => DATA_IN,
        COMMON_0_OUT => COMMON_0_OUT,
        COMMON_1_OUT => COMMON_1_OUT,
        COMMON_2_OUT => COMMON_2_OUT,
        A_OUT => A_OUT,
        B_OUT => B_OUT,
        C_OUT => C_OUT,
        D_OUT => D_OUT,
        E_OUT => E_OUT,
        F_OUT => F_OUT,
        G_OUT => G_OUT,
        DP_OUT => DP_OUT,
        OVERFLOW => OVERFLOW,

```

```

        TEST => TEST,
        RAMOUT => RAMOUT,
        ALUOUT => ALUOUT,
        RAMA => RAMA,
        RAMWR => RAMWR
    );

    CLOCK_process: process
    begin
        CLOCK <= '0';
        wait for 83ns;
        CLOCK <= '1';
        wait for 83ns;
    end process;

-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    lp1: for i in 4 to 4 loop
        lp2: for j in 2 to 2 loop
            TEST2 <= std_logic_vector((to_unsigned(1, 8) sll i)
+ j + 10) and std_logic_vector(to_unsigned(i, 8));
            ENTER_OP1 <= '1';
            ENTER_OP2 <= '1';
            CALCULATE <= '1';
            DATA_IN <= (others => '0');
            RESET <= '0';
            wait for CLKP;
            RESET <= '1';
            wait for CLKP;
            DATA_IN <= std_logic_vector(to_unsigned(i, 8)); --
A
            ENTER_OP1 <= '0';
            wait for CLKP;
            ENTER_OP1 <= '1';
            wait for CLKP;
            DATA_IN <= std_logic_vector(to_unsigned(j, 8)); --
B
            ENTER_OP2 <= '0';
            wait for CLKP;
            ENTER_OP2 <= '1';
            wait for CLKP;
            CALCULATE <= '0'; -- START CALCULATION

```

```

        wait for CLKP* 7;
        assert TEST = TEST2 severity FAILURE;
        wait for CLKP;
    end loop;
end loop;

    WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***

END;
```

 


Рис.8 – 7-сегментний індикатор

Переглянемо часову діаграму 7seg decoder.

Бачимо, що для вхідного числа  $00001111(2) = 15(10)$


Ми отримуємо такі значення(якщо значення не вказане, вважаємо його за одиницю):

COMM\_ONES = 0: A,C,D, F, G = 0, що відповідає числу 5

COMM\_DECS = 0: B,C = 0, що відповідає числу 1

COMM\_HUNDREDS = 0: A,B,C,D,E,F = 0, що відповідає числу 0

Отримуємо значення 015, що збігається з даним йому.

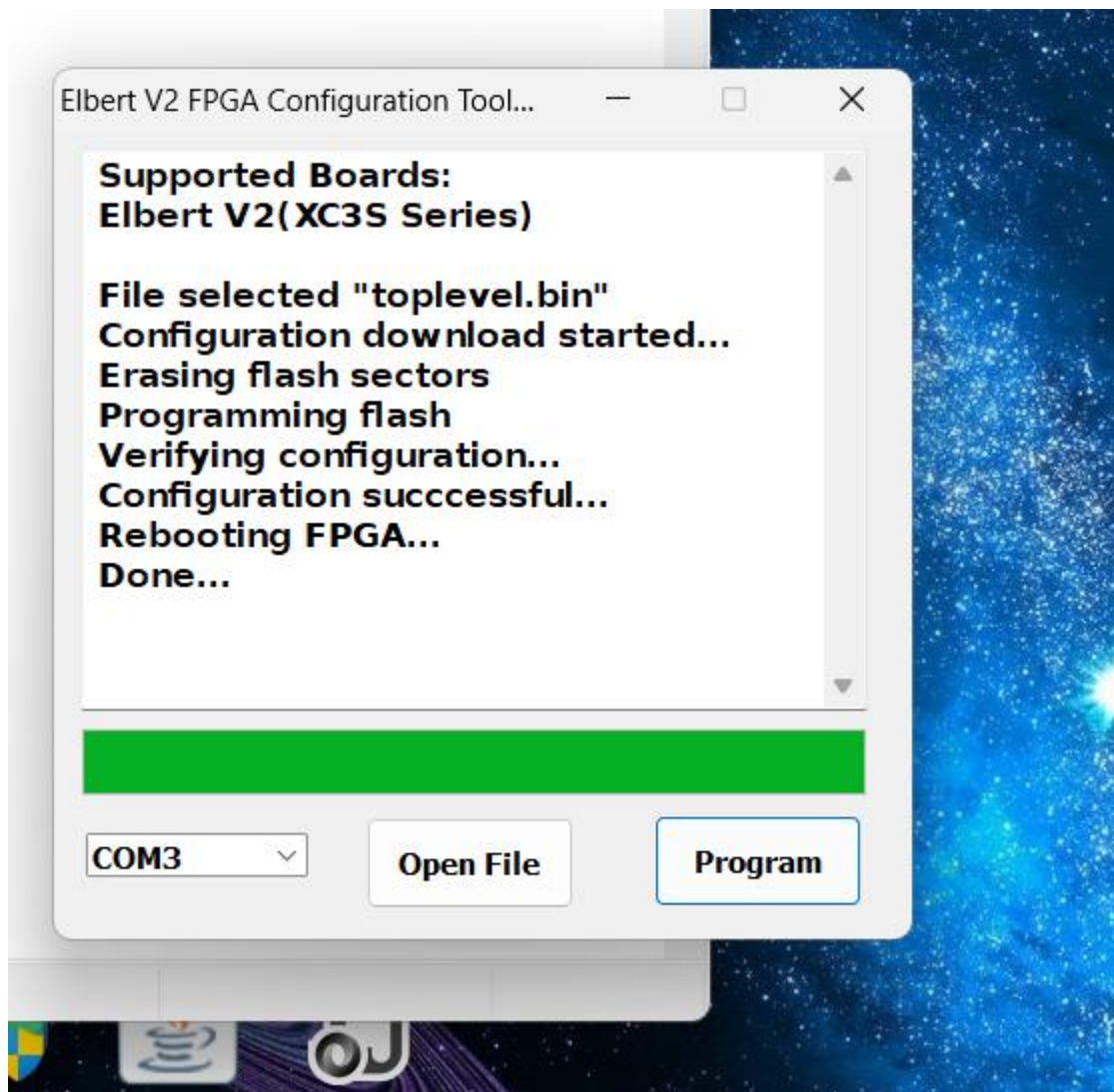

*Рис.9 – Успішна прошивка*

**Висновок:** Виконуючи дану лабораторну роботу я навчився реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.